

I B.Tech Regular Examinations, May/Jun 2006
ELECTRICAL CIRCUITS

(Common to Electrical & Electronic Engineering, Electronics & Control Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Find the voltage to be applied across AB in order to drive a current of 5A into the circuit by using star-delta transformation. Refer figure 1.

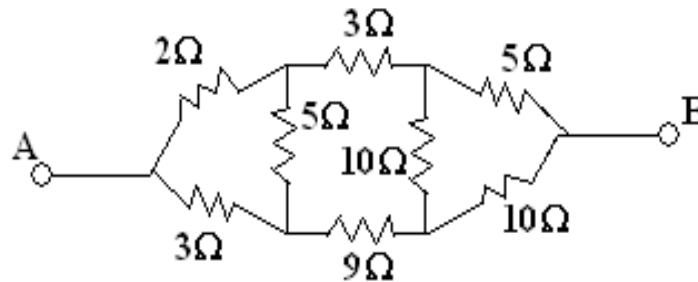


Figure 1:

- (b) Using Kirchoff's current law, find the values of the currents i_1 and i_2 in the circuit shown in figure 2. [8+8]

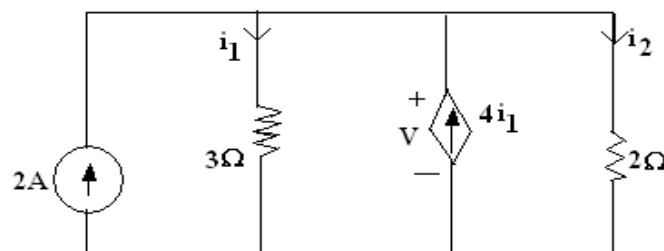


Figure 2:

2. (a) Define the following:
- Self inductance
 - Mutual Inductance
 - Static Induced e.m.f
 - Dynamically induced e.m.f.
- (b) Derive the relationship between the self, mutual inductances and coefficient of coupling.

- (c) Two similar coils connected in series gave a total inductance of 600 mH and when one of the coil is reversed, the total inductance is 300mH. Determine the mutual inductance between the coils and coefficient of coupling? [6+6+4]
3. (a) Bring out the differences between series and parallel resonance?
 (b) A series RLC circuit consists of resistance $R = 20\Omega$, inductance, $L=0.01\text{H}$ and capacitance, $C = 0.04 \mu\text{F}$. Calculate the frequency at resonance. If a 10 Volts of frequency equal to the frequency of resonance is applied to this circuit, calculate the values of V_C and V_L across C and L respectively. Find the frequencies at which these voltages V_C and V_L are maximum? [6+10]
4. (a) Three impedances each of $(3-j4) \Omega$ is connected in delta connection across a 3- ϕ , 230V balanced supply. Calculate the line and phase currents in the Δ connected load and the power delivered to the load?
 (b) In power measurement of 3- ϕ load connected by 3- ϕ supply by two wattmeter method, prove that $\tan \theta = \frac{-\sqrt{3}(w_1-w_2)}{(w_1+w_2)}$ for leading power factor loads. [8+8]
5. (a) For the circuit shown in figure 3, draw the graph and indicate tree.
 i. Branch
 ii. Node
 iii. Degree of a node
 iv. Links.
 (b) Using Nodal method, find the current through 5W resistor, in the following circuit. [6+10]

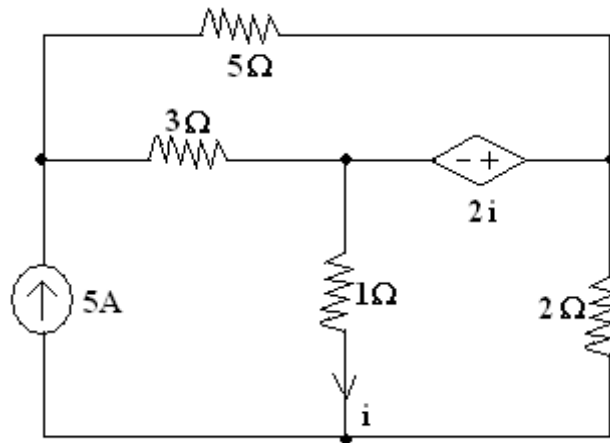


Figure 3:

6. (a) Explain the steps for solving a network problem using Thevenin's theorem.
 (b) Find the current I in the circuit shown in figure 4. [6+10]
7. Find $\vartheta_c(t)$ at $t = 0 +$ while the switching is done from x to y at $t = 0$. as shown in figure 5 [16]

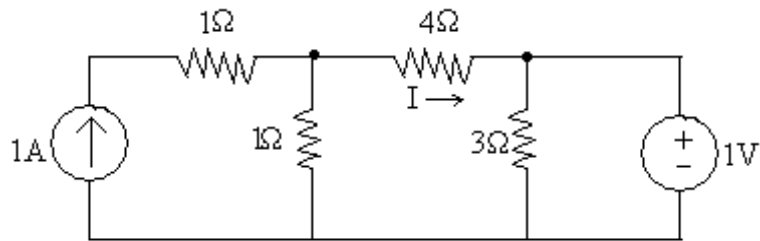


Figure 4:

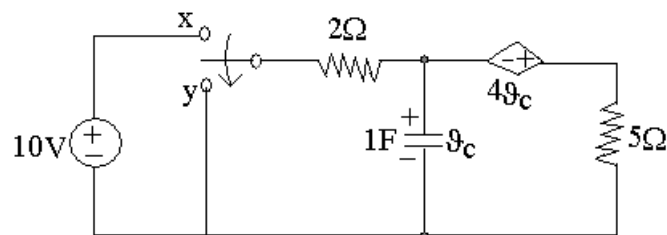


Figure 5:

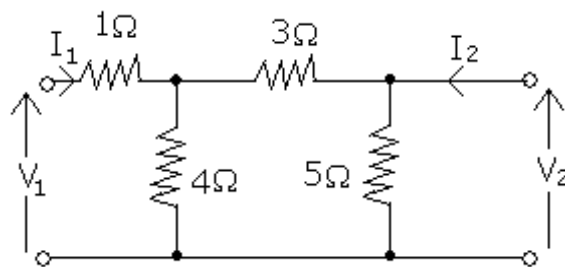


Figure 6:

Code No: R059010203

Set No. 1

8. (a) Determine the Z-parameter of the network shown in figure 6.
- (b) The y-parameters of a two port network are $y_{11}=0.6$ mho, $y_{22}=1.2$ mho and $y_{12}=-0.3$ mho.
- Determine the ABCD Parameters and
 - Equivalent Π network. [8+8]

**I B.Tech Regular Examinations, May/Jun 2006
ELECTRICAL CIRCUITS**

(Common to Electrical & Electronic Engineering, Electronics & Control Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) For the circuit shown in figure 1, find the current through 20Ω resistor?

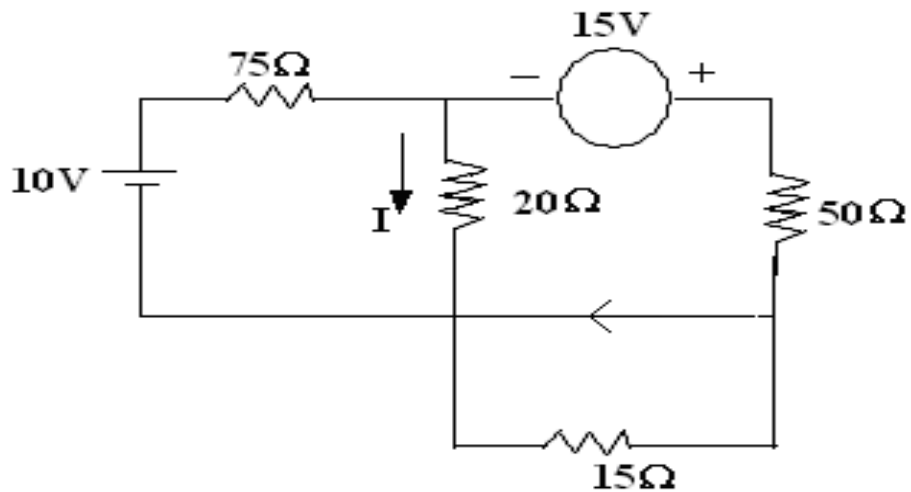


Figure 1:

- (b) Reduce the network shown in figure 2, to a single loop network by successive source transformation, to obtain the current in the 12Ω resistor. [8+8]

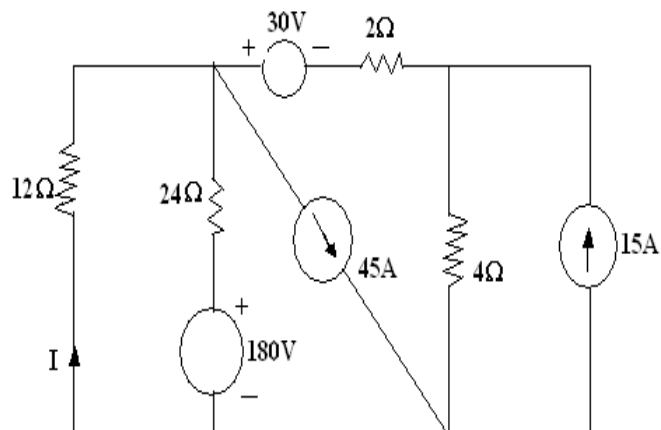


Figure 2:

2. (a) Write short notes on dot convention used in magnetically coupled coils.
- (b) In the network shown in figure 3, $L_1=1\text{H}$, $L_2=2\text{H}$, $M=1.2\text{H}$. Assuming the inductance coils to be ideal, find the amount of energy stored after 0.1 sec of the circuit connected to a d.c.source of 10V. [6+10]

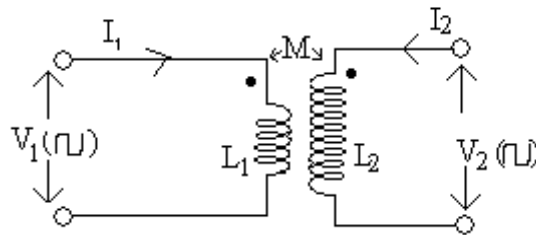


Figure 3:

3. (a) Explain the concept of
- Susceptance and
 - Admittance
- (b) An inductive coil takes 10A and dissipates 1000 watts when connected to a supply of 250v, 25Hz. Calculate.
- the impedance
 - the effective resistance
 - reactance
 - the inductance
 - power factor. Also, Draw the vector diagram. [6+10]
4. (a) A balanced 3-ph star connected load of 150 Kw takes a leading current of 100A with a line voltage of 1100 V, 50Hz. Find the circuit constants of the load per phase?
- (b) Three equal star connected inductors takes 8Kw at P.f of 0.8 when connected to 460V, 3- ϕ , 3 wire supply. Find the line currents, if one conductor is short circuited. [6+10]
5. (a) Define the following and explain by taking an example.
- Node
 - Tree
 - Sub graph
 - Loop
 - Links
 - Directed graph.
- (b) Find the fundamental tie-set and cut-set matrix for the graph and for the tree shown in the figure 4. [9+7]

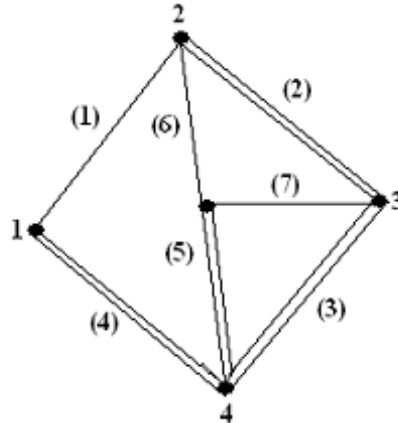


Figure 4:

6. (a) State and explain compensation theorem.
 (b) In the network shown in figure 5, find the value of Z_L so that the power transfer from the source is maximum. Also find P_{max} . [8+8]

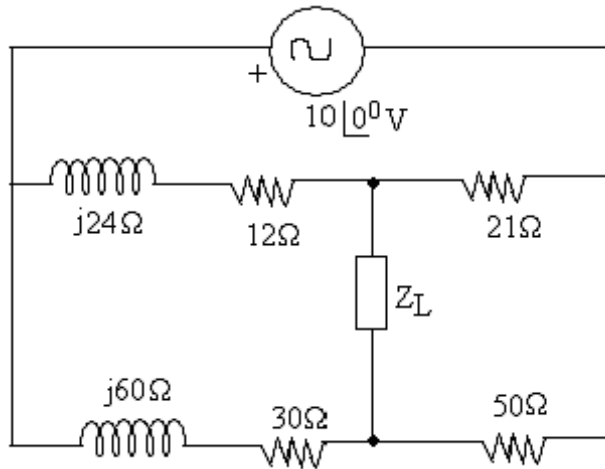


Figure 5:

7. (a) A dc voltage of 100V is applied in the circuit shown in figure 6 and the switch is kept open. The switch K is closed at $t = 0$. Find the complete expression for the current.
 (b) A dc voltage of 20V is applied in a RL circuit where $R = 5\Omega$ and $L = 10H$. Find [8+8]
 i. The time constant
 ii. The maximum value of stored energy.
8. (a) Find the Z-parameters for the network shown in figure 7.
 (b) For the h parameter equivalent network shown in figure 8 find the voltage gain load resistance is R_L . [6+10]

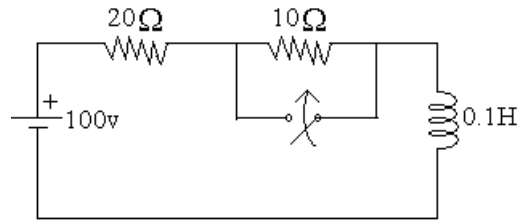


Figure 6:

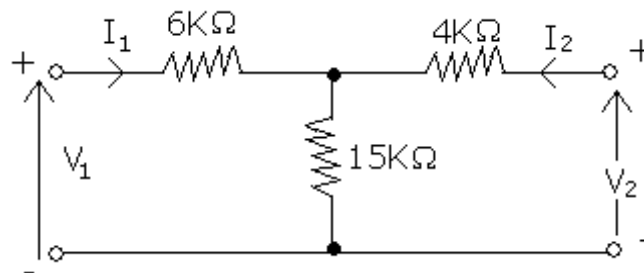


Figure 7:

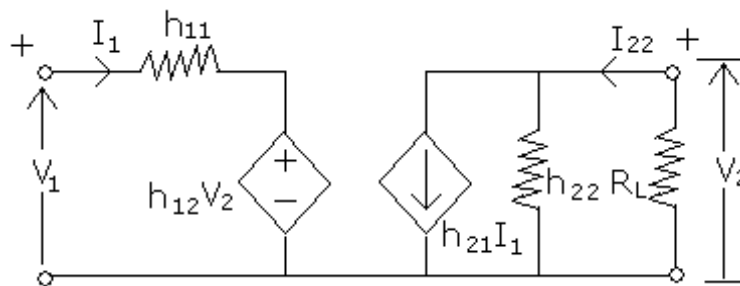


Figure 8:

Code No: R059010203

Set No. 2

**I B.Tech Regular Examinations, May/Jun 2006
ELECTRICAL CIRCUITS**

(Common to Electrical & Electronic Engineering, Electronics & Control Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) For the circuit shown in figure 1, find the current through 20Ω resistor?

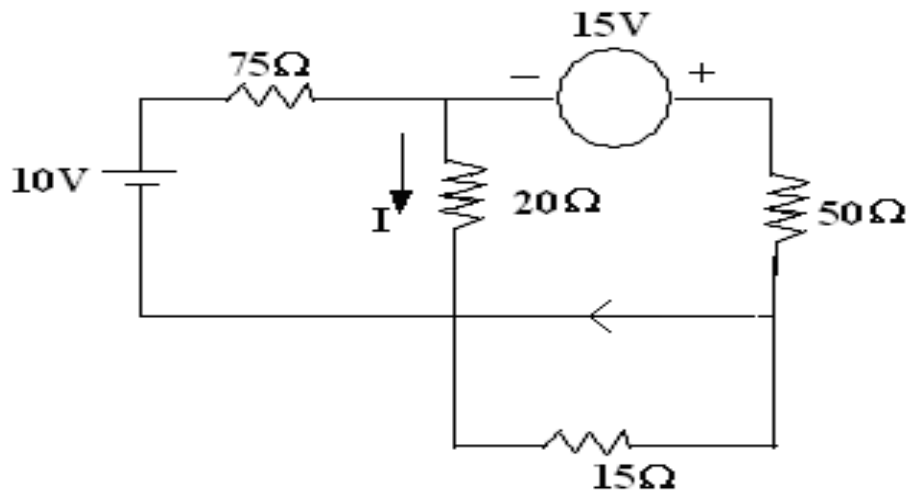


Figure 1:

- (b) Reduce the network shown in figure 2, to a single loop network by successive source transformation, to obtain the current in the 12Ω resistor. [8+8]

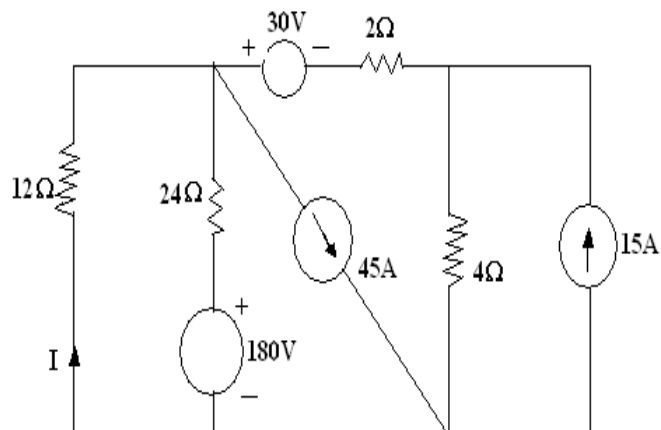


Figure 2:

2. (a) Explain
- Statically induced e.m.f and
 - Dynamically induced e.m.f
- (b) The combined inductance of two coils connected in series is 0.6H or 0.1H , depending upon the relative directions of the currents in the coils. If one of the coils when isolated has a self inductance of 0.2H , Calculate
- Mutual inductance, and
 - The Coefficient of coupling.
- (c) Explain the terms
- MMF
 - Reluctance. [6+6+4]
3. (a) Draw the current, impedance and admittance loci for an R L series circuit having fixed resistance but variable reactance.
- (b) figure 3 shows a series parallel circuit. Find
- admittance of each branch
 - admittance between points b and g.
 - impedance between points b and g.
 - total circuit impedance
 - total current and power factor
 - currents in each branch. [6+10]

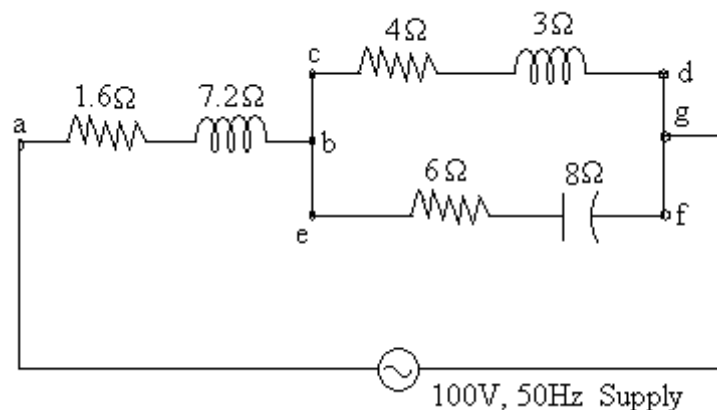


Figure 3:

4. (a) Three identical resistances are connected in a star fashion against a balanced three phase voltage supply. If one of the resistance is removed, how much power is to be reduced?
- (b) A 3-phase load has a resistance of 10Ω in each phase and is connected in
- star and

- ii. delta against a 400V, 3-phase supply. Compare the power consumed in both the cases.
- (c) What is the difference between RYB phase sequence with RBY phase sequence? [6+6+4]
5. (a) Define the following and explain by taking an example.
- Branch
 - Node
 - Path
 - Sub graph
 - Tree
 - Degree of a node.
- (b) Draw the oriented graph of the network shown in figure 4 and write the cut set matrix. [9+7]

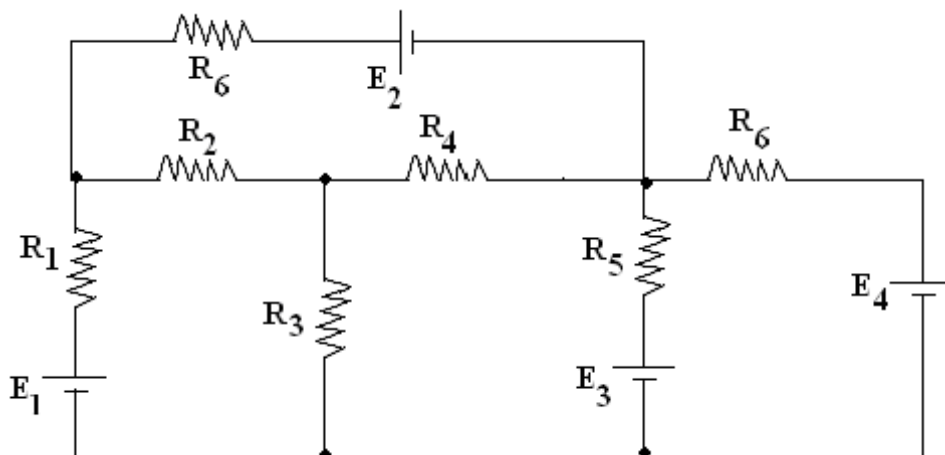


Figure 4:

6. (a) State and explain the Millmann's theorem.
- (b) Find the current in the 6Ω resistor using Superposition theorem. as shown in figure 5 [6+10]
7. (a) A dc voltage of 100V is applied in the circuit shown in figure 6 and the switch is kept open. The switch K is closed at $t = 0$. Find the complete expression for the current.
- (b) A dc voltage of 20V is applied in a RL circuit where $R = 5\Omega$ and $L = 10H$. Find [8+8]
- The time constant
 - The maximum value of stored energy.
8. (a) In a T network shown in figure 7, $Z_1 = 2\angle 0^\circ$, $Z_2 = 5\angle -90^\circ$, $Z_3 = 3\angle 90^\circ$, find the Z-parameters.

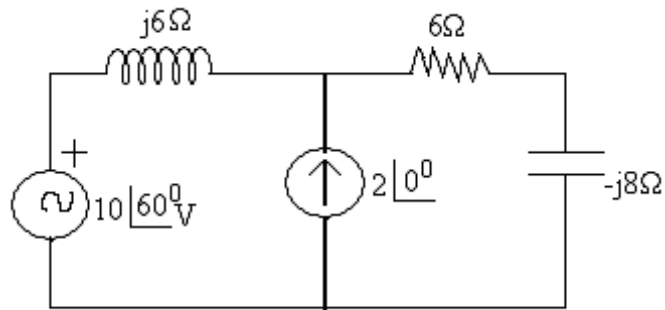


Figure 5:

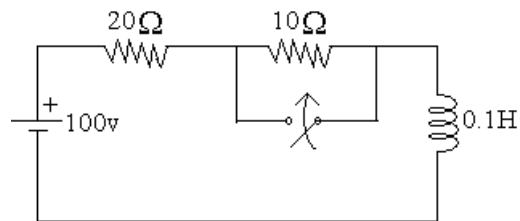


Figure 6:

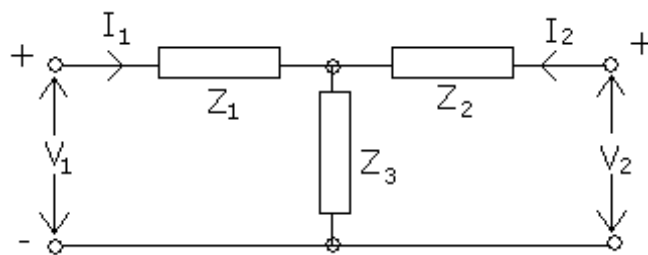


Figure 7:

Code No: R059010203

Set No. 3

- (b) Z-parameters for a two port network are given as $Z_{11}=25\Omega$, $Z_{12}=Z_{21}=20\Omega$,
 $Z_{22}=50\Omega$. Find the equivalent T-network. [8+8]

I B.Tech Regular Examinations, May/June 2006
ELECTRICAL CIRCUITS

(Common to Electrical & Electronic Engineering, Electronics & Control Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain
 - i. KCL
 - ii. KVL
 - iii. Practical current source
 - iv. Practical voltage source.
- (b) A 20V battery with an internal resistance of 5 ohms is connected to a resistor of x ohms. If an additional resistance of 6Ω is connected across the battery, find the value of x , so that the external power supplied by the battery remain the same. [8+8]
2. (a) Explain the following terms:-
 - i. Magnetic circuit
 - ii. Permeability
 - iii. Magneto motive force
 - iv. Reluctance.
- (b) A cast steel structure is made of a rod of square section $2.5\text{cm} \times 2.5\text{cm}$ as shown in figure 1. What is the current that should be passed in a 500 turn coil on the left limb, so that a flux of 2.5mwb is made to pass in the right limb. Assume permeability as 750 and neglect leakage. [8+8]

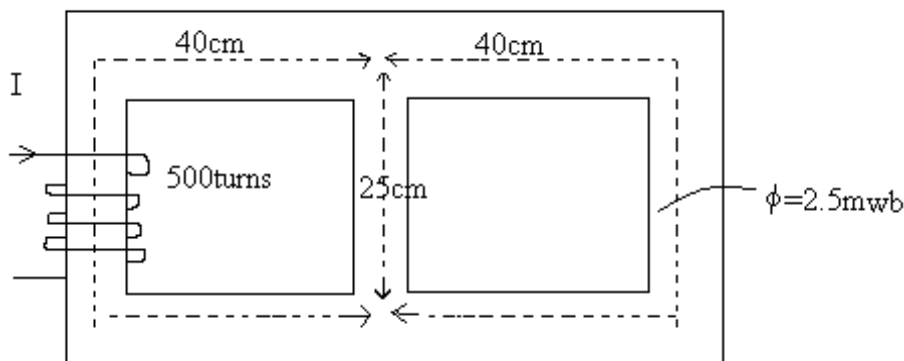


Figure 1:

3. (a) Derive the expression for power in a $1-\phi$ A.c circuits.

- (b) In the circuit shown in figure 2, Calculate.
- The total impedance
 - The total current
 - Power factor
 - The total S,P and Q
 - The total admittance. Also, draw vector diagram.

[6+10]

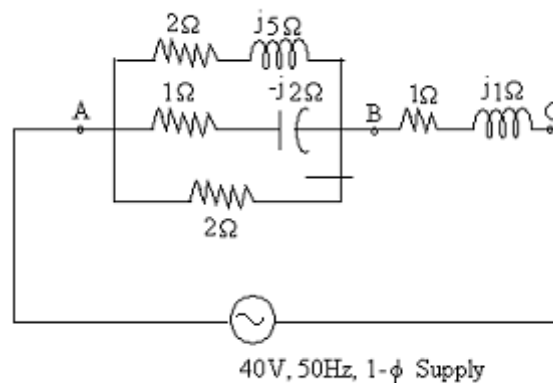


Figure 2:

- Two resistors each of 100Ω are connected in series. The phases a and c of a three phase 400V supply are connected to the two ends and phase b is connected to the junction of the two resistors. Find the line currents.
 - Derive the expressions for wattmeter readings in two wattmeter method with balanced star connected load. How do you calculate the power factor of the balanced load from wattmeter readings? [8+8]
- Define the following and explain by taking an example.
 - Node
 - Tree
 - Sub graph
 - Loop
 - Links
 - Directed graph.
 - Find the fundamental tie-set and cut-set matrix for the graph and for the tree shown in the figure 3. [9+7]
- State and explain compensation theorem.
 - In the network shown in figure 4, find the value of Z_L so that the power transfer from the source is maximum. Also find P_{max} . [8+8]
- In the figure 5, the switch is close at position 1 at $t = 0$. At $t = 0.5$ m sec. The switch is moved to position 2. Find the expression for the current in both the conditions and sketch the transient. [16]

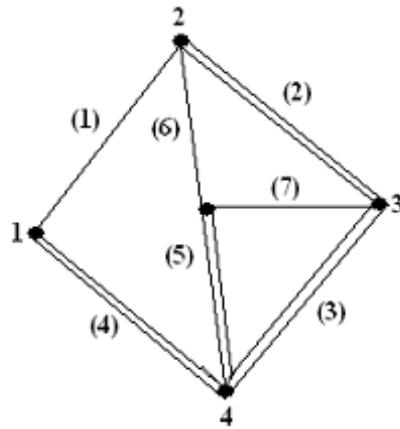


Figure 3:

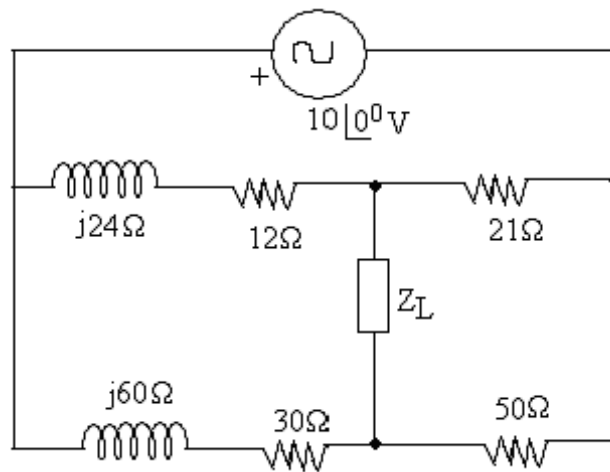


Figure 4:

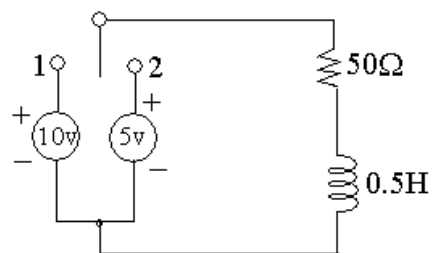


Figure 5:

8. Determine Y-Parameters of the network shown in figure 6.

[16]

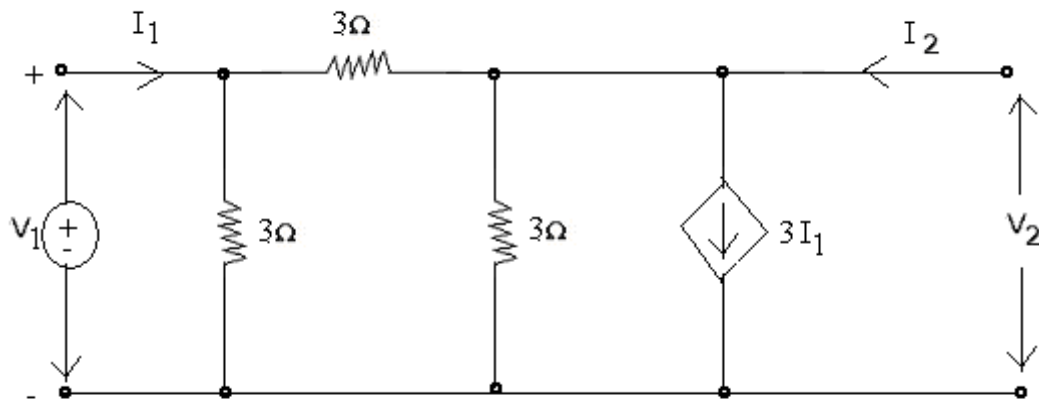


Figure 6:
